


Electronics Option - Operational Amplifier (Op-amp) Circuits

Apparatus

‘Locktronics’ Circuit Board + Components
Signal Generator
Connecting Wires

‘Tops’ Stabilised Power Supply
Cathode Ray Oscilloscope

Theory and circuit diagrams

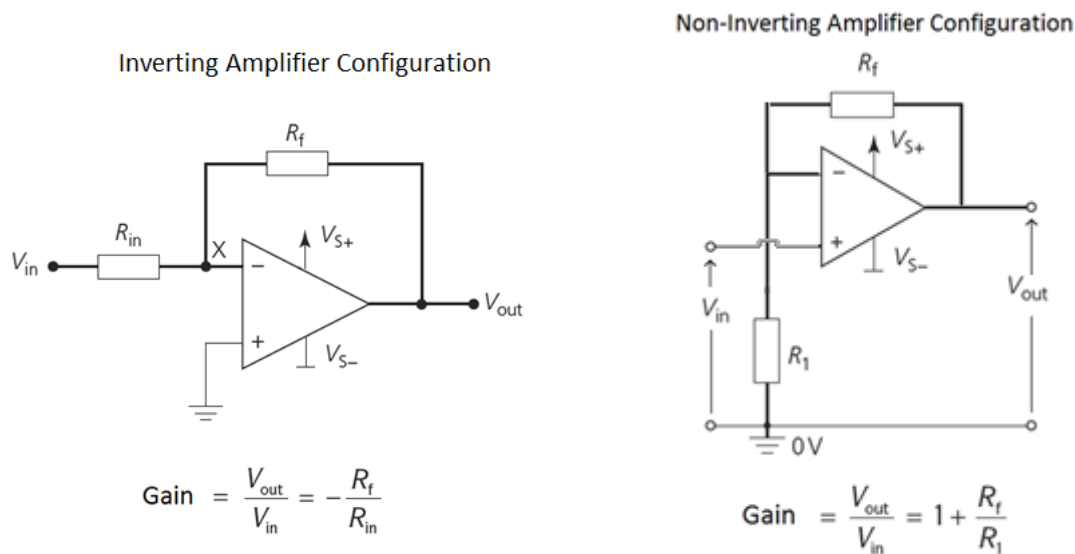

Method

First set up the inverting amplifier circuit using $R_f = R_{\text{in}} = 10 \text{ k}\Omega$. Note that V_{S+} and V_{S-} should be connected to the $\pm 15 \text{ V}$ output for the ‘Tops’ supply and the 0 V terminal should be connected in common with the green earth terminal for the CRO and Signal Generator. You should use 2 channels on the CRO to observe both input and output signals.

Using a suitable input signal of about 500 Hz, sketch the input and output traces produced and measure the peak-to-peak input and output voltages.

Repeat the process with the same input resistor, but with $R_f = 33 \text{ k}\Omega$.

Now construct the non-inverting amplifier circuit using $R_f = R_1 = 10 \text{ k}\Omega$ and perform the same measurements with this circuit. Repeat the measurements with $R_f = 33 \text{ k}\Omega$.

Analysis

For each of your circuits, calculate the gain of the amplifier ($V_{\text{out}}/V_{\text{in}}$).

Use the gain formula given to compare the expected gain with the measured gain for each circuit.