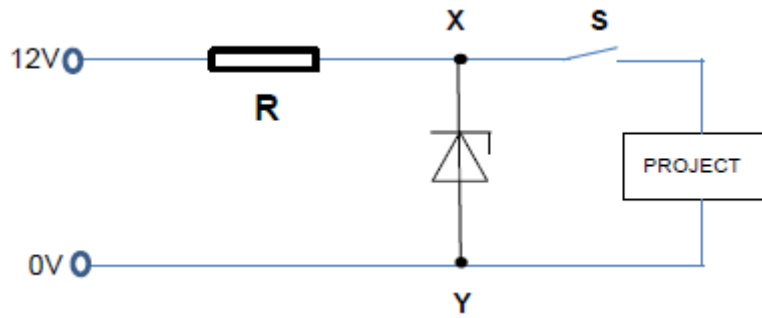


Practice electronics Paper Mark Scheme

M1.(a)



1 mark for Zener symbol  
1 mark for orientation

2

(b) (i)  $80\text{mA} + 5\text{mA} = 85\text{mA}$   
*Answer - 1*

1

(ii)  $12\text{V} - 5.1\text{V} = 6.9\text{V}$   
*Calculation and answer - 1*

1

(iii)  $R = 6.9\text{V} / 85\text{mA} = 81\Omega$   
*Calculation and answer - 2*

2

(c) (i)  $P = V^2 / R_P = (6.9 \times 6.9) / 75 = 0.64\text{W}$   
Hence P is approx. 0.6W  
*Calculation and answer - 2*


2

(ii)  $I = V / R \quad I = 6.9 / 75 \quad I = 92\text{mA}$   
*Calculation and answer - 2*

2

[10]

M2.(a)

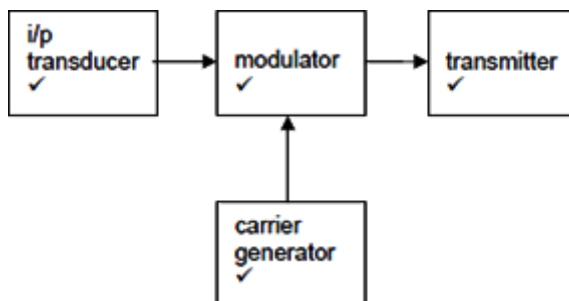

4

(b) (i) carrier generator ✓

1

(ii) use of  $f = \frac{1}{2\pi\sqrt{LC}}$  ✓  
 $\frac{1}{2\pi\sqrt{10^{-7} \times 5 \times 10^{-12}}}$  ✓  
 225 MHz ✓

3

(c) calc leading to  $\lambda = 1.32\text{m}$  ✓  
 $1.33 \div 2 = 0.66\text{m}$  ✓

2

[10]

**M3.(a)** Choice of 20kΩ ✓  
 pot div calculation ✓  
 8V ✓

3

(b) upper half the value of lower ✓  
 in range 1kΩ to 10kΩ ✓  
 preferred values 1kΩ and 2kΩ, or 1.8kΩ and 3.6kΩ etc ✓

3

(c) (i) +12V or high ✓

1

(ii) 0V or low ✓

1

[8]

**M4.(a)** (i) inverting (amplifier) (1)

1

(b) use of  $V_{\text{out}} = (-) \frac{R_f}{R_i} \times V_{\text{in}}$  (1)

$$= (-) \frac{120}{30} \times 0.5 = -2.0 \text{ V (1)}$$

2

(c) (i)  $V_{\text{peak (input)}} = 2.0 \times \sqrt{2} = 2.8(3) \text{ V (1)}$

(ii) input trace (A): sinusoidal with  $T = 20 \text{ ms (1)}$   
 and peak = 2.8 V (1)

for output voltage,  $V_{\text{peak (out)}} = (-) \frac{120}{30} \times 2.8(3) = (\pm)11.3 \text{ (V) (1)}$

(allow C.E. for value of  $V_{\text{peak (input)}}$  from (i))

trace B: inversion w.r.t. trace A (1)  
 same period as trace A (1)  
 flat region (saturates) at  $\pm 5 \text{ V (1)}$

max 6

[9]

**M5.(a)**  $D = C + B$

$$E = \overline{A} \quad 1$$

$$G = \overline{A+B} \quad 1$$

3

(b)

INPUTS			INTERMEDIATE OUTPUTS		
C	B	A	D	E	G
0	0	0	0	1	1
0	0	1	0	0	0
0	1	0	1	1	0
0	1	1	1	0	0
1	0	0	1	1	1
1	0	1	1	0	0
1	1	0	1	1	0
1	1	1	1	0	0

*2 marks for each of correct columns D & G  
1 mark for column E*

5  
(Total 8 marks)